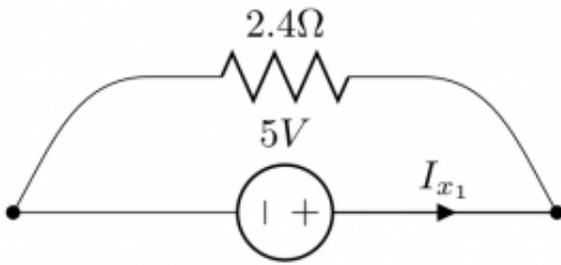


$$4\Omega || 6\Omega = \frac{4 \times 6}{4+6} = 2.4\Omega$$




www.solved-problems.com


So using Ohm's law:

$$I_{x1} = \frac{5V}{2.4\Omega} = 2.083A$$

To continue solving the circuit with the Superposition method, we should make the voltage source zero and find the contribution of the current source on I_x . Making voltage source means replacing it with a short circuit. Similar to the current source, you may memorize this by remembering that you need to make the source value (here: voltage) equal to zero and to force zero voltage drop between two points you need to connect them.

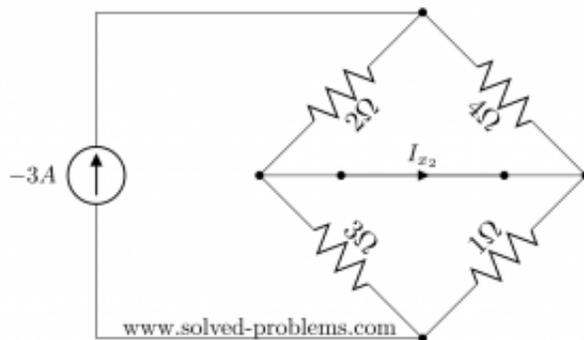

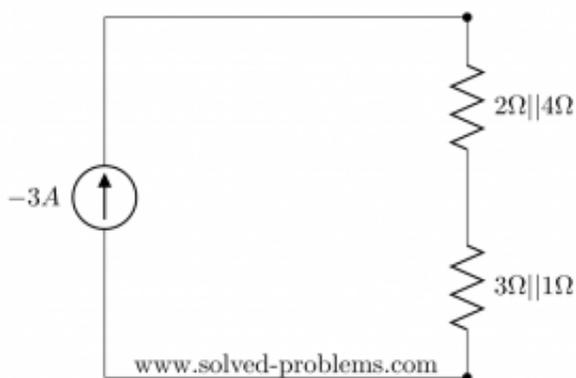For a moment forget I_x and concentrate on finding current of resistors. If we have the current of resistors, we can easily apply KCL and find I_{x2} . So, 4Ω and 2Ω are parallel and also 3Ω and 1Ω are parallel:



$$4\Omega || 2\Omega = \frac{4 \times 2}{4+2} = \frac{4}{3}\Omega$$

$$3\Omega || 1\Omega = \frac{3 \times 1}{3+1} = \frac{3}{4}\Omega$$

Now, we can find their voltage drops:

$$V_{4\Omega || 2\Omega} = \frac{4}{3} \times -3A = -4V$$


$$V_{3\Omega || 1\Omega} = \frac{3}{4} \times -3A = -2.25V$$

Please note that the voltage drop on $4\Omega || 2\Omega$ is the same as 4Ω and 2Ω voltage drops, because the circuits are equivalent and all are connected to the same nodes. The same statement is correct for $3\Omega || 1\Omega$ voltage drop and 3Ω and 1Ω voltage drops. So

$$V_{4\Omega} = V_{2\Omega} = V_{4\Omega || 2\Omega} = -4V$$

$$V_{3\Omega} = V_{1\Omega} = V_{3\Omega || 1\Omega} = -2.25V$$

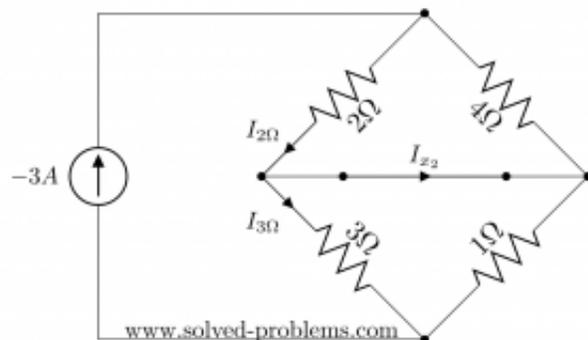To find I_{x_2} all we need is to write KCL at one of the nodes:



$$-I_{2\Omega} + I_{x_2} + I_{3\Omega} = 0$$

$$\rightarrow I_{x_2} = I_{2\Omega} - I_{3\Omega}$$

$I_{2\Omega}$ and $I_{3\Omega}$ can be found using Ohm's law:

$$I_{2\Omega} = \frac{V_{2\Omega}}{2\Omega} = \frac{-4}{2} = -2A$$

$$I_{3\Omega} = \frac{V_{3\Omega}}{3\Omega} = \frac{-2.25}{3} = -0.75A$$

Therefore,

$$I_{x_2} = -1.25A$$

And

$$I_x = I_{x_1} + I_{x_2} = 2.083 - 1.25 = 0.8333A$$

Now, replace 1Ω resistor with a 6Ω one and solve the circuit using superposition method. Let me now your answer below in the comments section.

Solution sheet

[Superposition method Circuit with two sources Solved Problems](#)

Download