



left to right:

$$+V_x + R_1 \times I_{R_1} + V_x = 0$$

$$\rightarrow 2V_x = -R_1 \times I_{R_1}$$

$$\rightarrow V_x = -\frac{R_1 \times I_{R_1}}{2}$$

But what is  $I_{R_1}$ ?  $R_1$  is in series with the current source; they have only one node shared and there is no other element connected there. This means that all current of  $I_S$  must pass through  $R_1$ . Therefore,  $I_{R_1} = I_S = 2A$ .

If we apply this to the equation above, we have

$$V_x = -\frac{R_1 \times I_{R_1}}{2} \rightarrow V_x = -5V.$$

Since no current passing through  $R_2$  we can easily see that  $V_{OC} = V_x$ . If it is not clear, you could find this by applying KVL to the right hand side loop:

$$-V_x + R_2 \times I_{R_2} + V_{OC} = 0$$

$$\rightarrow -V_x + R_2 \times 0 + V_{OC} = 0$$

$$\rightarrow V_{OC} = V_x = -5V$$

## Short circuit current

Next, we need to find the short circuit current. It means we need to connect terminals of the network and calculate the current passing through the connection:

Doing so, we get a circuit with two loops. **It is very important to note that all values might be changed and we are not allowed to use values/formulas of the open circuit voltage calculation.** Just forget all and analyze the new circuit and calculate short circuit current  $I_{SC}$ .

Please note that the mesh currents (loop currents for not-shared portion of loops) are as shown above. For the left hand side loop it is equal to the current of the current source as current sources enforce their current to go through all elements in series with them. For the right hand side loop it is  $I_{SC}$  and there is no benefit in defining a new label for current.

KVL for the left loop:

$$+V_x + R_1 \times I_{R_1} + V_x = 0$$

Again, here the current of  $I_{R_1}$  is equal to  $I_S$  and  $I_{R_1} = I_S = 2A$ .

$$+V_x + 5 \times 2 + V_x = 0$$

$$\rightarrow V_x = -5V.$$

We get the same value for  $V_x$ . This is not a general rule and value could be different.

For the right hand side loop:

$$-V_x + R_2 \times I_{SC} = 0$$

$$I_{SC} = \frac{V_x}{R_2} = -\frac{5}{3}A$$

## Thevenin's and Norton's Equivalent Networks

The only thing left is to calculate  $R_{th}$  which can be easily found by

$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{-5}{-\frac{5}{3}} = 3\Omega$$

Thevenin's Equivalent Network

$$V_{th} = V_{OC} = -5V$$

$$R_{th} = 3\Omega$$

Norton's Equivalent Network

$$I_{no} = I_{SC} = -\frac{5}{3}A$$

$$R_{no} = R_{th} = 3\Omega$$

Now, assume that a  $2V$  voltage source is connected to the terminals of this network, what would be its current?


Copyright 2019 Solved Problems

[www.solved-problems.com](http://www.solved-problems.com)

Processing math: 10%