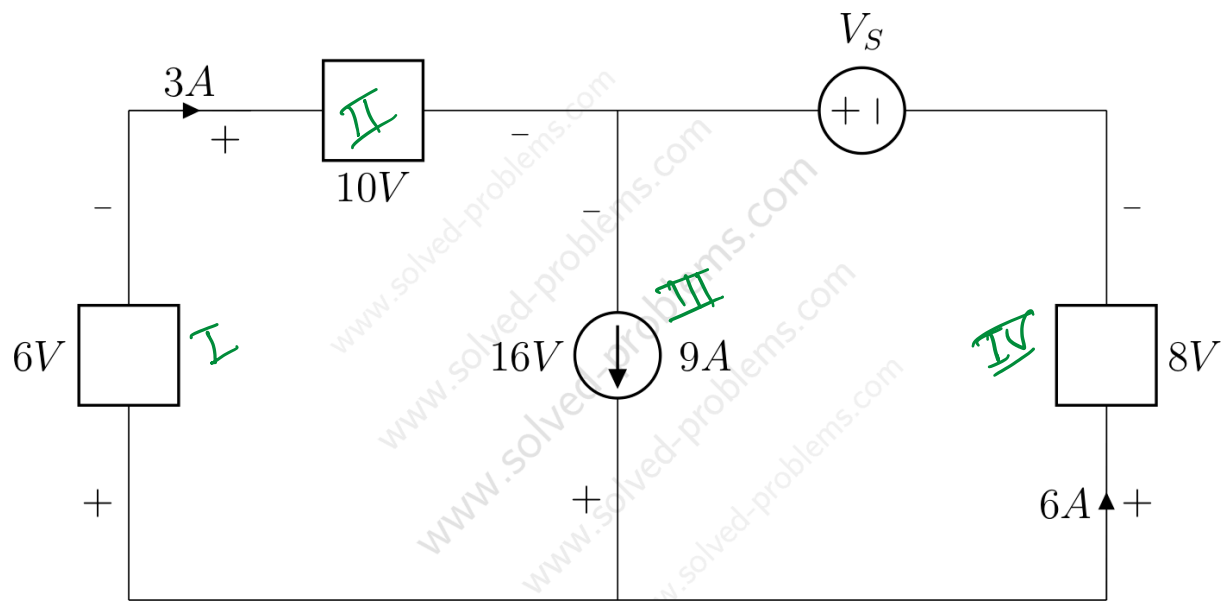



Is the source V_s absorbing or supplying power, and how much?



Positive sign convention

$P > 0 \rightarrow$ Absorbing power

$P < 0 \rightarrow$ Supplying power

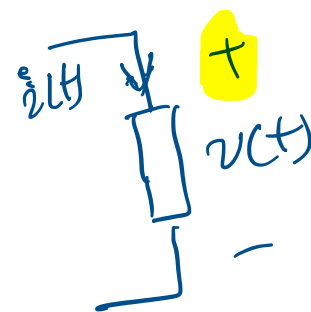


I $P_I = 3A \times 6V = 18W > 0$ Absorbing

II $P_{II} = 3A \times 10V = 30W > 0$ Absorbing

III $P_{III} = -9A \times 16V = -144W < 0$ Supplying

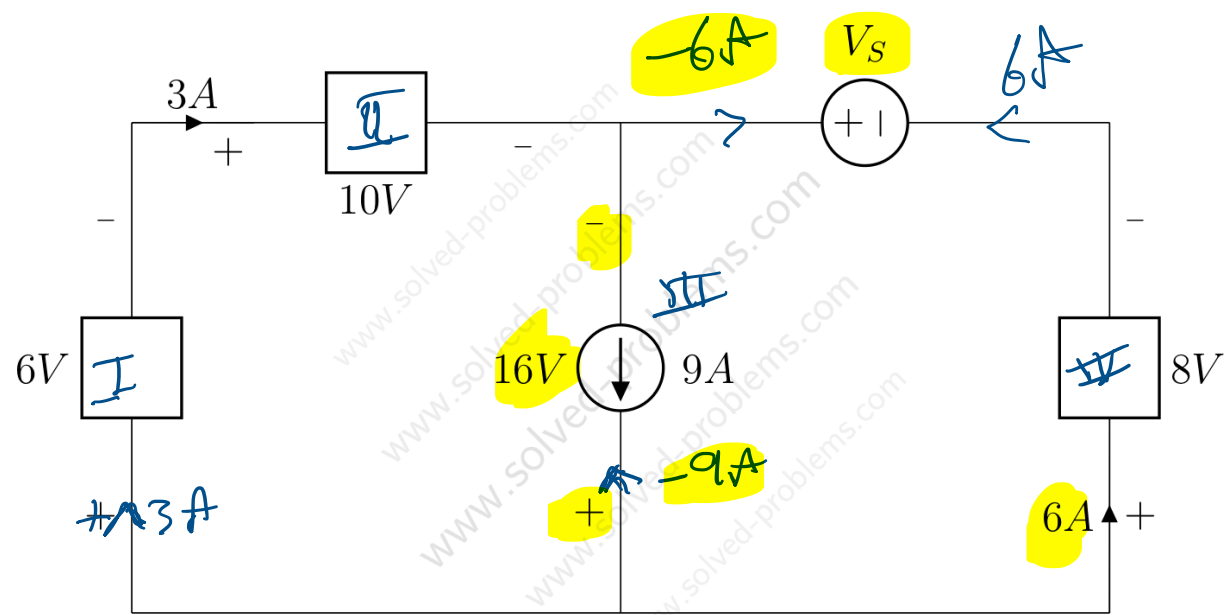IV $P_{IV} = 6A \times 8V = 48W > 0$ Absorbing



Absorbing: $18W + 30W + 48W = 96W$

Supplying: $144W$

$P_{Vs} : 144 - 96 = 48$ absorbing

$P_I + P_{II} + P_{III} + P_{IV} + P_{Vs} = 0 \rightarrow$

$P_{Vs} = 48W > 0$
Absorbing

$P_{Vs} = -6A \times V_s = 48W \rightarrow V_s = \frac{48W}{-6A} = -8V$